

$$S_{11} = \frac{Z_r - Z_0}{Z_r + Z_0}$$

$$Z_r = \frac{1}{i\omega C_c} + \left( \frac{1}{R_r} + \frac{1}{i\omega L_r} + i\omega C_r \right)^{-1}$$

$$\Rightarrow S_{11} = \frac{1 - \omega^2 L_r \left[ C_r + C_c \left( 1 - \frac{Z_0}{R_r} \right) \right] + i\omega \left[ \frac{L_r}{R_r} - Z_0 C_c (1 - \omega^2 L_r C_r) \right]}{1 - \omega^2 L_r \left[ C_r + C_c \left( 1 + \frac{Z_0}{R_r} \right) \right] + i\omega \left[ \frac{L_r}{R_r} + Z_0 C_c (1 - \omega^2 L_r C_r) \right]}$$

At resonance impedance vanishes:

$$\frac{1}{i\omega_0 C_c} + \frac{1}{i\omega_0 C_r + \frac{1}{i\omega_0 L_r}} = 0$$

$$\text{resonance freq} \Rightarrow \omega_0 = 1/\sqrt{L_r(C_r + C_c)}$$

Assuming  $R_r \gg Z_0$ , on resonance:

$$|S_{11}(\text{res})| = \left| \frac{\frac{L_r}{Z_0 R_r C_r} - \frac{\chi^2}{1+\chi}}{\frac{L_r}{Z_0 R_r C_r} + \frac{\chi^2}{1+\chi}} \right|,$$


ratio of  $\frac{\text{coupling } C}{\text{resonator } C}$

$$\text{with } \chi = \frac{C_c}{C_r}$$

$Z$ : characteristic

impedance of resonator

$$= \left| \frac{\frac{Z^2}{Z_0} \frac{1}{R_r} - \frac{\chi^2}{1+\chi}}{\frac{Z^2}{Z_0} \frac{1}{R_r} + \frac{\chi^2}{1+\chi}} \right|$$

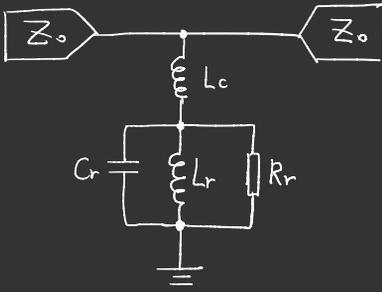

$$S_{11} = \frac{Z_r - Z_0}{Z_r + Z_0} \quad C_c \rightarrow -\frac{1}{\omega^2 L_c}$$

$$Z_r = i\omega L_c + \left( \frac{1}{R_r} + \frac{1}{i\omega L_r} + i\omega C_r \right)^{-1}$$

$$\Rightarrow S_{11} = \frac{-\omega^2 L_r C_r + \frac{L_r}{L_c} \left( 1 - \frac{Z_0}{R_r} \right) + i \left[ \omega \frac{L_r}{R_r} + \frac{Z_0}{\omega L_c} \left( 1 - \omega^2 L_r C_r \right) \right]}{-\omega^2 L_r C_r + \frac{L_r}{L_c} \left( 1 + \frac{Z_0}{R_r} \right) + i \left[ \omega \frac{L_r}{R_r} - \frac{Z_0}{\omega L_c} \left( 1 - \omega^2 L_r C_r \right) \right]}$$

At resonance impedance vanishes:

$$i\omega_0 L_c + \frac{1}{i\omega_0 C_r + \frac{1}{i\omega_0 L_r}} = 0$$

$$\text{resonance freq} \Rightarrow \omega_0 = \sqrt{\frac{1}{C_r} \left( \frac{1}{L_c} + \frac{1}{L_r} \right)}$$

Assuming  $R_r \gg Z_0$ , on resonance:

$$|S_{11}(\text{res})| = \left| \frac{\frac{L_r}{Z_0 R_r C_r} - \frac{1}{\chi(x+1)}}{\frac{L_r}{Z_0 R_r C_r} + \frac{1}{\chi(x+1)}} \right| ,$$

ratio of  $\frac{\text{coupling } L_c}{\text{resonator } L_r}$

$$\text{with } \chi = \frac{L_c}{L_r}$$


$Z$ : characteristic

impedance of resonator

$$= \left| \frac{\frac{Z^2}{Z_0} \frac{1}{R_r} - \frac{1}{\chi(x+1)}}{\frac{Z^2}{Z_0} \frac{1}{R_r} + \frac{1}{\chi(x+1)}} \right|$$

length  $\uparrow$   $L_c \uparrow$

diameter  $\downarrow$   $L_c \uparrow$


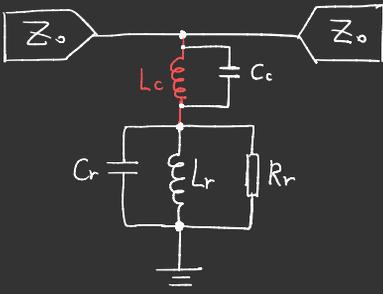


$$S_{11} = \frac{Z_r - Z_0}{Z_r + Z_0}$$

length  $\uparrow$   $L_c \uparrow$   
diameter  $\downarrow$   $L_c \uparrow$

$$Z_r = \left[ \left( \frac{1}{i\omega C_c} \right)^{-1} + (i\omega L)^{-1} \right]^{-1} + \left( \frac{1}{R_r} + \frac{1}{i\omega L_r} + i\omega C_r \right)^{-1}$$

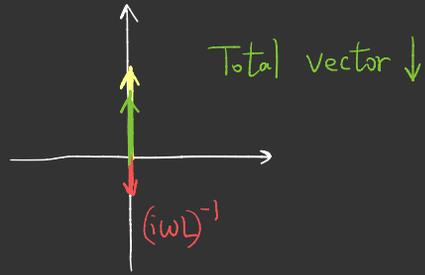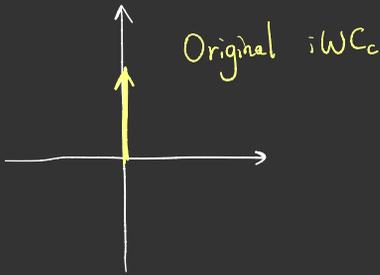$I_s$  actually substituting  $\frac{1}{i\omega C_c} \rightarrow \left[ \left( \frac{1}{i\omega C_c} \right)^{-1} + (i\omega L)^{-1} \right]^{-1}$



$I_s$  actually increasing  $C_c$ !  $C_c' = C_c + \frac{1}{\omega^2 L}$

